
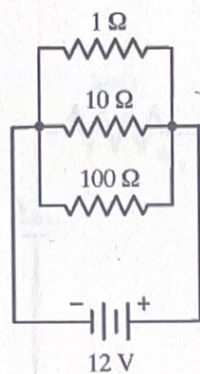


11. Determine the total resistance of each circuit below.

a) Answer to 3 significant figures.

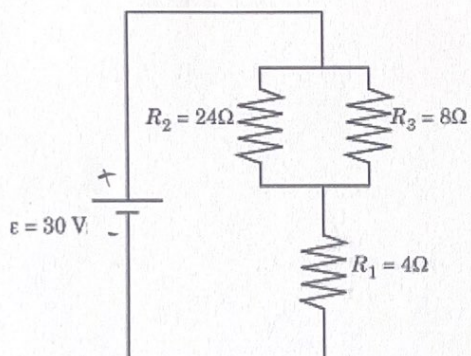

b) Answer to 3 significant figures.



does a circuit breaker protect your home?

SIDES

SIDES

Physics 11

c) Answer to 2 decimal places.

